

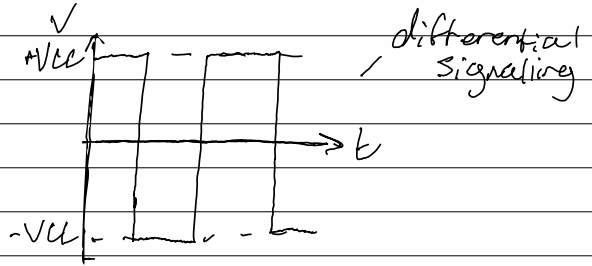
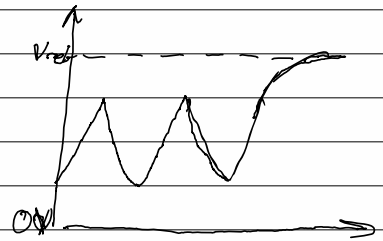

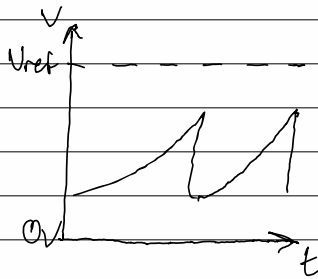
# Analog Measurements


Digital Signals: Are voltages that cycle between 0V and  $+V_{CC}$  volts (5V = CMOS/Arduino) or  $\pm V_{CC}$



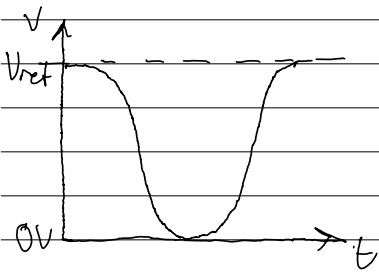Analog Signals: Are voltages that can be between 0V and  $V_{ref}$  volts and are typically waveforms (sine, triangle, sawtooth)



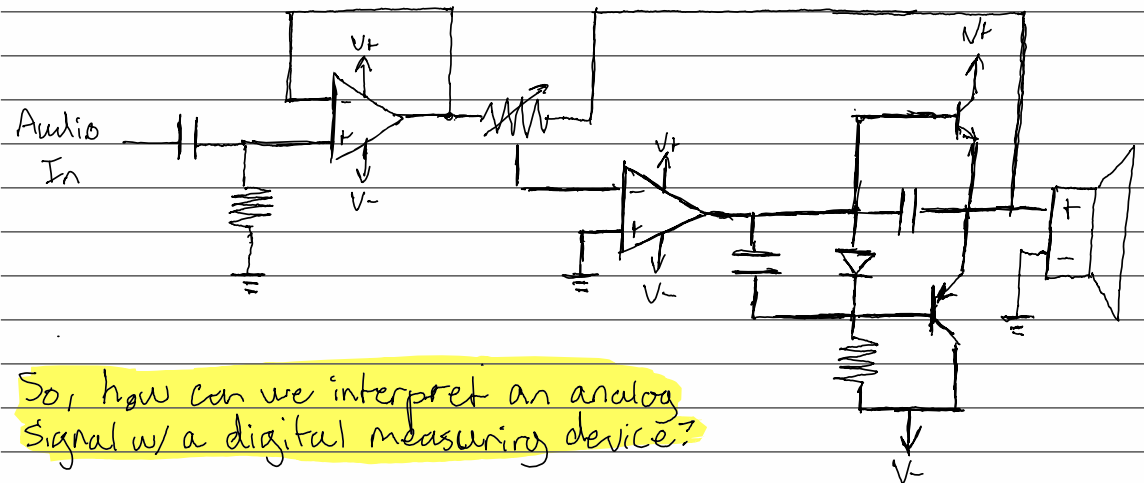Inherently, most circuits w/o a dedicated electronic controller




So, how can we interpret an analog signal w/ a digital measuring device?

## Analog Measurements (cont.)
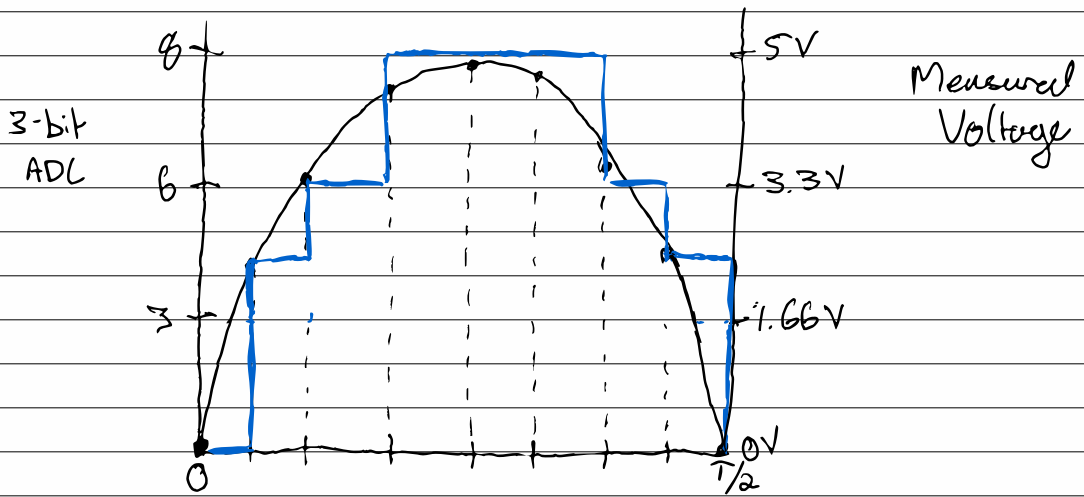
### Analog to Digital Conversion

• Analog-to-digital converters (ADCs) sample an analog signal to create discrete points that represent the waveform



ADC value reported is a ratio of system voltage, resolution, and measured voltage.

$$\frac{\text{ADC resolution [bins]}}{\text{System Voltage [V]}} = \frac{\text{ADC Reading [bins]}}{\text{Measured Voltage [V]}}$$

In example case,

$$\frac{8 [\text{bins}]}{5 \text{ V}} \times \frac{x}{3.3 \text{ V}} \Rightarrow \frac{8 \cdot 3.3}{5} = x = 5.28 \Rightarrow 6$$


In Arduino case (10-bit ADC)

$$\frac{1024 [\text{bins}]}{5 \text{ V}} \times \frac{x}{3.3} = \frac{1024 \cdot 3.3}{5} = x = 675.84 \Rightarrow 676$$

# Analog Measurements (cont.)
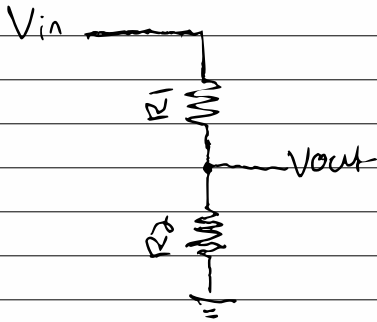
## Voltage Divider


Voltage dividers lower an input voltage down to a different value depending on the value of two resistors



$$V_{out} = V_{in} \cdot \frac{R_2}{R_1 + R_2}$$


Ex: Battery voltage monitor

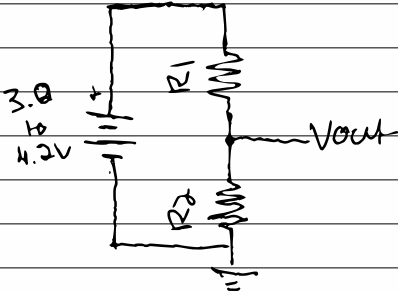$V_{io} = 3.3V$ ,  $V_{bat} (max) = 4.2V$ . Want 4.2V to map to 3.3V




$$3.3 = 4.2V \cdot \frac{R_2}{R_1 + R_2} \quad \text{For simplicity, } R_2 = 10k\Omega$$
$$= 4.2V \cdot \frac{10 \times 10^3}{R_1 + 10 \times 10^3}$$
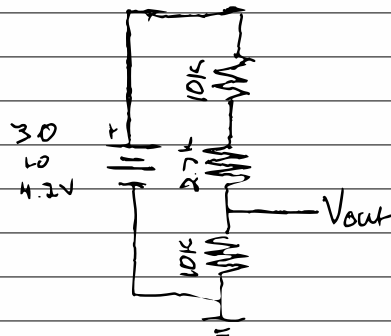
$$\frac{3.3}{4.2 \times 10^3} = \frac{1}{R_1} \Rightarrow R_1 = \frac{4.2 \times 10^3}{3.3} = 12.7 \times 10^3 \Omega$$
$$12.7k = \underbrace{10k + 2.7k}_{\text{more common}} \quad \downarrow \text{Rare!}$$



# Analog Measurements (cont.)

## Wheatstone Bridge


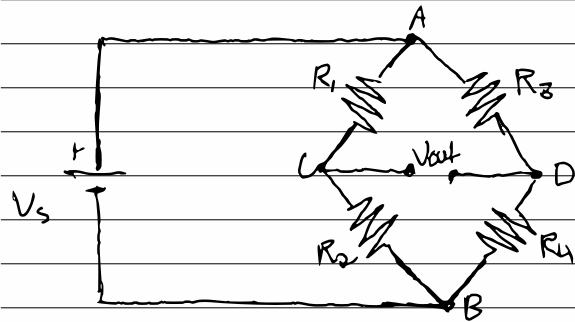


The wheatstone bridge is a way to measure and calibrate analog resistive sensors

It compares an unknown resistance to a known resistance and can allow for very low resistances (milli-ohms) to be measured.

Amplifier circuits downstream of the bridge's output ( $V_{out}$ ) can allow a digital controller to read real analog values.

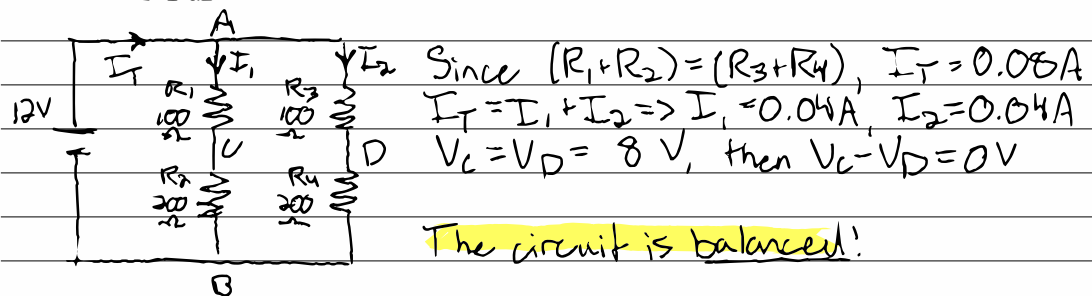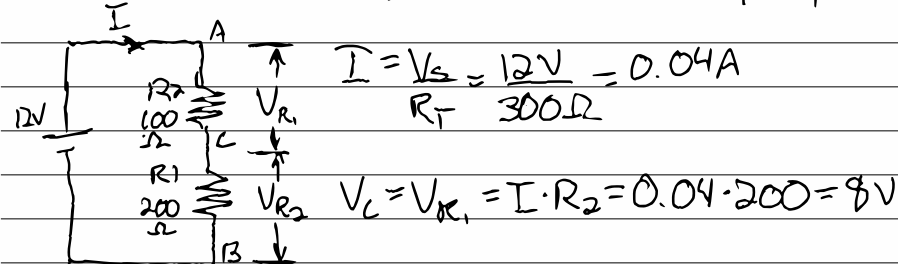
This circuit is a hybrid series-parallel circuit as there are two series circuits of two resistors each, in parallel



The circuit is balanced!

# Analog Measurements (cont.)

## Wheatstone Bridge (cont.)

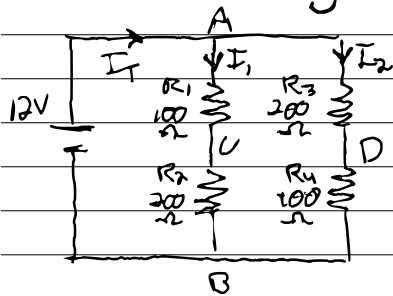

Since resistor totals are the same, current will remain the same.


$$V_P = I_2 \cdot R_4 = 0.04 \cdot 100 = 4 \text{ V}$$

$$V_C \neq V_P \therefore V_{CD} = V_C - V_P = 8 - 4 = 4 \text{ V}$$

$\therefore$  Bridge is unbalanced

The resistance ratio of these parallel arms,  $ACB/ADB$  results in a voltage difference across C and D.

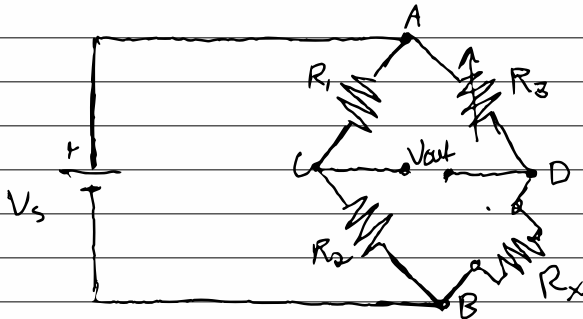So, we can keep  $R_1$  and  $R_2$  known, easy constants, make  $R_3$  variable, and use  $R_4$  to be an unknown but non-zero value.



We can set the system into a known steady, "calibrated" state, and use the variable resistor,  $R_3$ , to "balance" the bridge.

$$\frac{R_1}{R_2} = \frac{R_3}{R_x} = 1 \approx \text{"Balanced"}$$

$$V_{out} = (V_C - V_P) = V_{in} \left( \frac{R_2}{R_1 + R_2} - \frac{R_x}{R_3 + R_x} \right) = 0 \rightarrow \text{when balanced}$$

Where  $R_1$  and  $R_2$  are known or preset values.

$$R_2 = R_x$$

$$R_1 + R_2 = R_3 + R_x$$

$$R_2(R_3 + R_x) = R_x(R_1 + R_2)$$

$$R_2 R_3 + R_2 R_x = R_x R_1 + R_x R_2$$


$$\boxed{\frac{R_2 R_3}{R_1} = R_x}$$

## Analog Measurements (cont.)
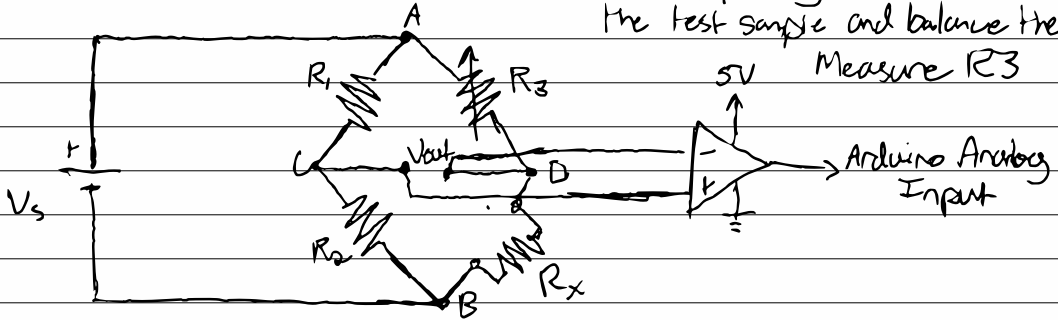
### Wheatstone Bridge (cont.)

Ex: Load cell (Strain gauge)

Start by placing the load cell on the test sample and balance the bridge  
Measure  $R_3$



- Arduino will detect the voltage difference across C and D through the OP-Amp and analog input
- Can calculate  $R_x$  using circuit theory.
- Correlate  $R_x$  w/ sensor Ohms/mil or Ohms/mm value to calculate the elongation.